

Making Circuits Work

- 1 Use the words in the boxes to fill in the gaps in the sentences below.


SWITCH BREAK ON COMPLETE
ELECTRICITY BREAK OFF

A circuit which has a in it will not allow to flow through it.

A device called a can be used to or a circuit so that other devices can be switched or .

- 2 The following circuits do not work. Explain why and what needs to be done to make them work.

a)

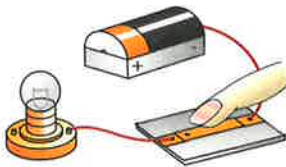

Why it doesn't work:

What needs to be done:


b)



Why it doesn't work:

What needs to be done:

c)

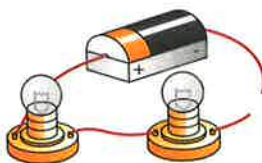

Why it doesn't work:

What needs to be done:

d)



Why it doesn't work:

What needs to be done: