


Physical Processes 3

1 Draw the symbols for the following:



a)	b)	c)
d)	e)	f)

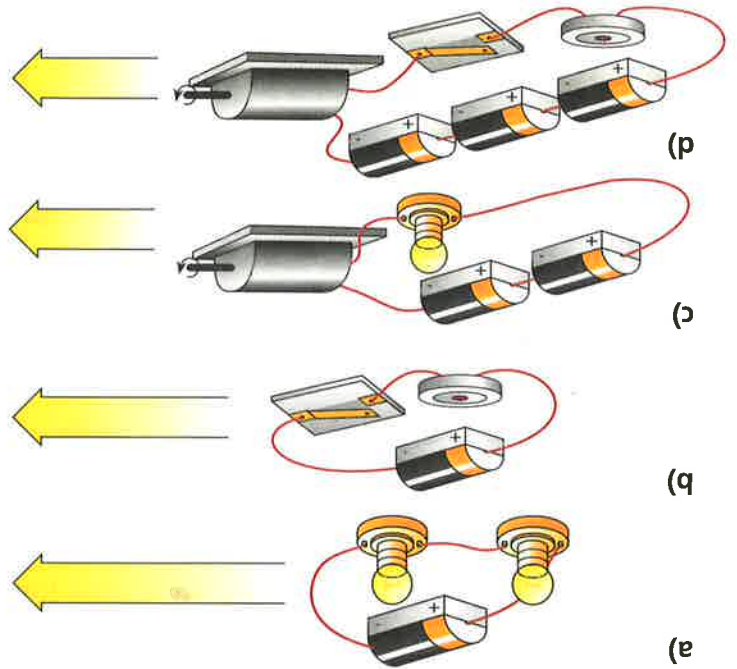2 Draw a circuit diagram for each of the following circuits. Make sure you use a ruler.



3 Below are two circuit diagrams. For each circuit draw the circuit.

