

Make the circuit work

Circuit Diagram



What are the components in this circuit?

Will electricity flow through this circuit?


☐ Yes ☐ No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.



Circuit Diagram

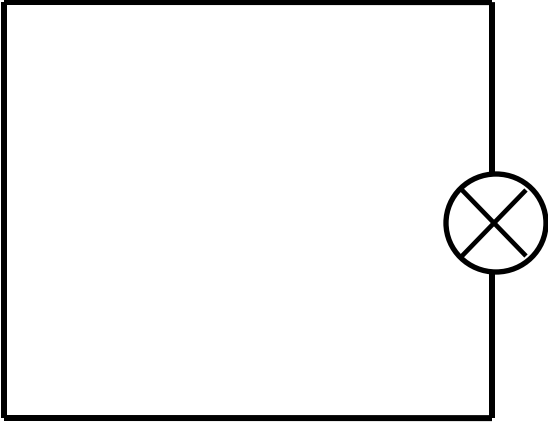

What are the components in this circuit?

Will electricity flow through this circuit?


☐ Yes ☐ No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.



Circuit Diagram

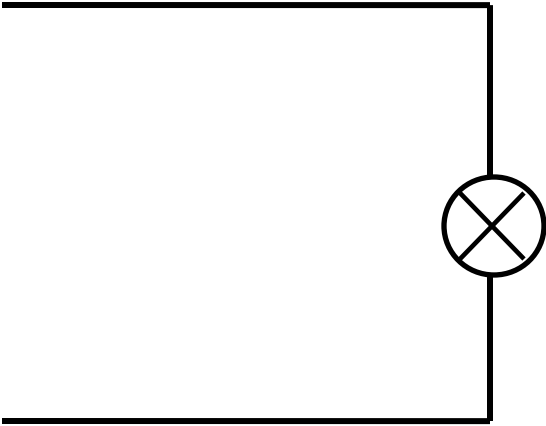

What are the components in this circuit?

Will electricity flow through this circuit?


☐ Yes ☐ No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.



Circuit Diagram

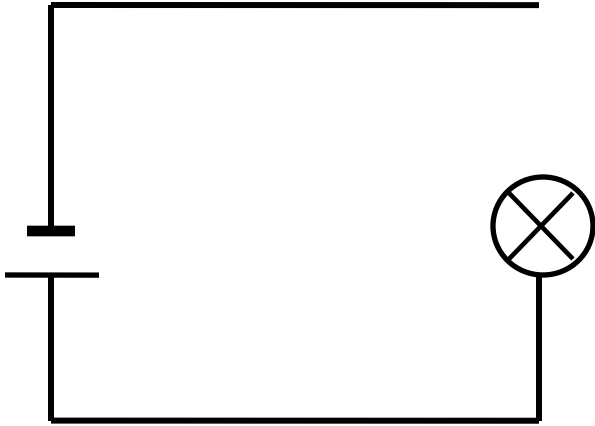

What are the components in this circuit?

Will electricity flow through this circuit?


☐ Yes ☐ No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.

A large, empty rounded rectangle for drawing a diagram to complete the circuit.

Circuit Diagram

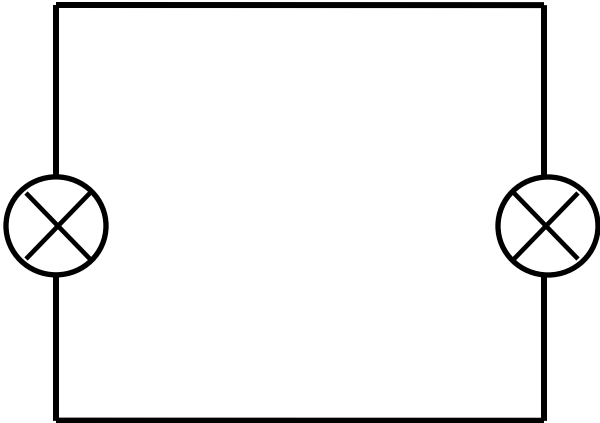

What are the components in this circuit?

Will electricity flow through this circuit?

☐


Yes

☐

No

What is missing from this circuit to make it work?

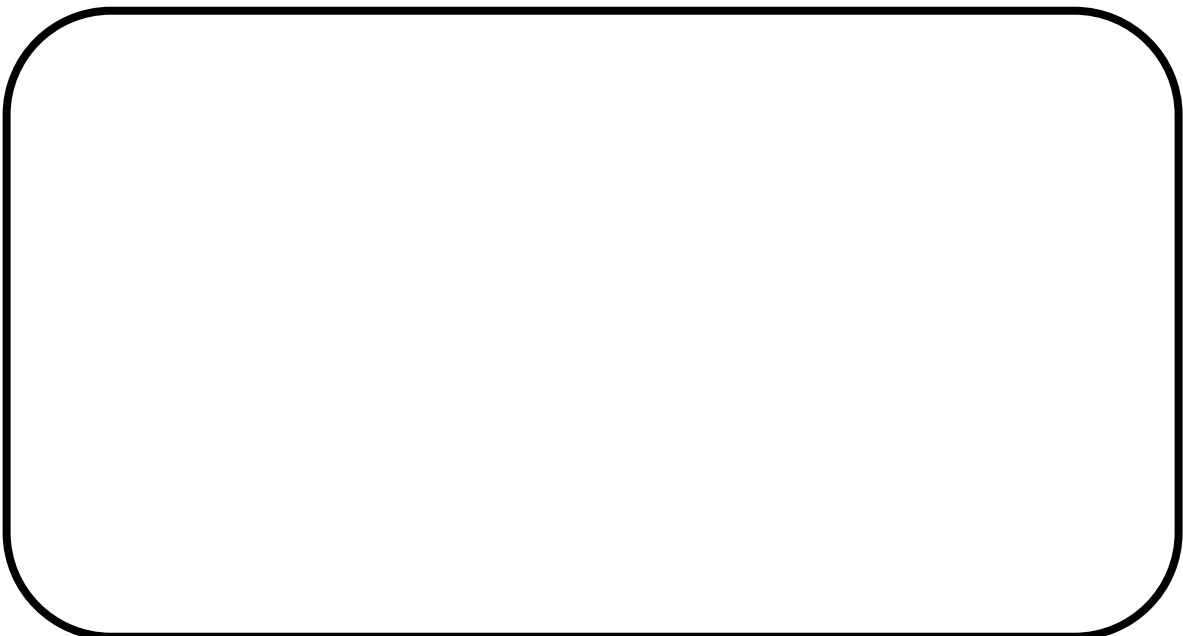Draw a diagram to complete the circuit that will allow the electricity to flow.



Circuit Diagram



What are the components in this circuit?

Will electricity flow through this circuit?

☐

Yes

☐

No

What is missing from this circuit to make it work?

Draw a diagram to complete the circuit that will allow the electricity to flow.

A large, empty rounded rectangle with a thick black border, intended for the student to draw a diagram that completes the circuit.